


Measuring Internal Resistance

Charlie Coleman

Jose Antonio Conde


Aparna Shekar

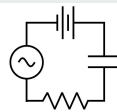Junior Design
ECE 3090
MDH 1018
April 17, 2018




Goal

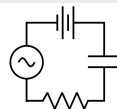- To find the internal resistance of a 7.2 V rechargeable battery




Outline

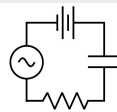
- Our approach
 - First approach
 - Second approach
 - Final approach
- Procedure
 - Experiment
 - Formulas and theorems
 - Calculations
- Results
- Conclusions



Our approach: First

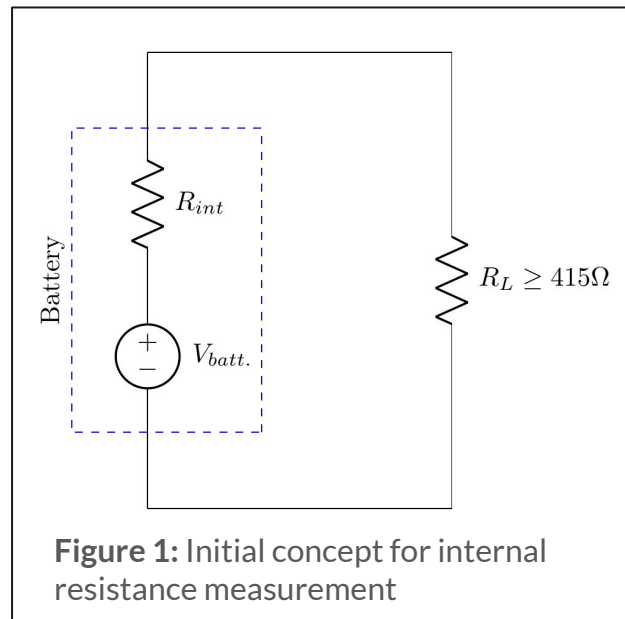- Battery in series with a resistor
- The voltage measured and compared it with its theoretical value
- Problems:
 - The battery couldn't draw enough current
 - The resistances had to have a large enough power rating to handle the voltage going through it



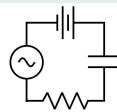

Our Approach: Second

- Combination of AC source with a transformer
 - Step up current
 - Step down voltage
- Battery in series with AC source of 7.2 V (peak)
- Initial calculations based on 8:1 transformer
- Problems:
 - Inconsistent internal resistances (ranged from 18-400 Ω) due to inductance of the transformer



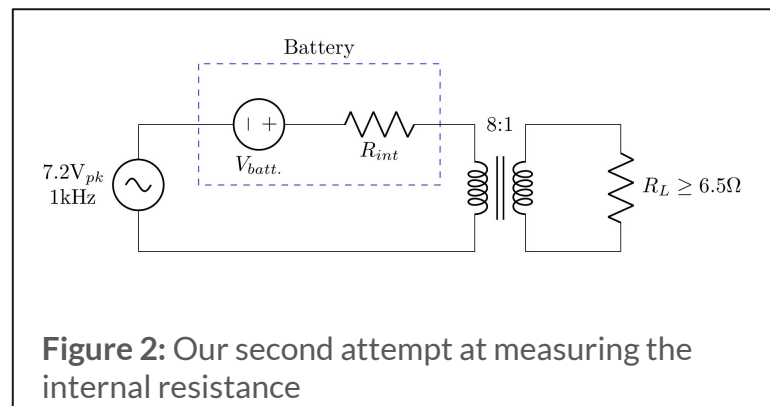


Figure 2: Our second attempt at measuring the internal resistance

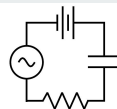

Our Approach: Final

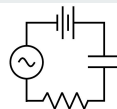- Capacitors act like an open circuit with DC voltage
 - Allowed use of smaller resistors
- Needed to ensure capacitor was capable of 7.2V
 - Used 470 μ F 16V capacitor
- Changed frequency and observed effects
 - Found internal impedance of battery



Circuit Diagrams for Final Approach

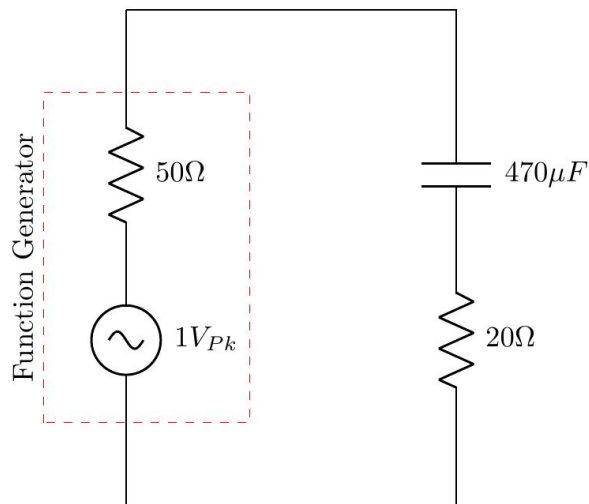


Figure 3: The circuit used to find the impedance of the circuit without the battery



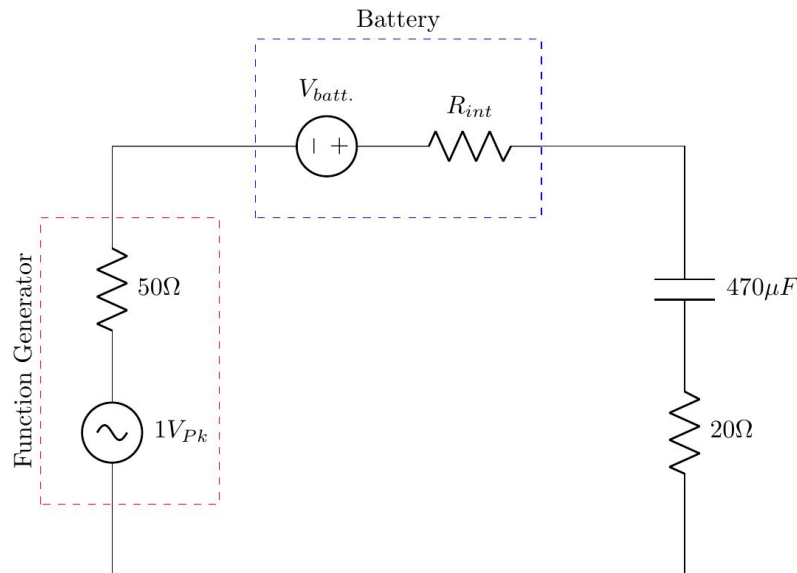


Figure 4: The circuit used to find the internal resistance of the battery

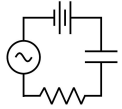


Procedure

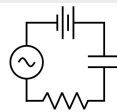1. Constructed **Figure 3**, but replaced the 20Ω resistor with a $1.3k\Omega$ resistor
2. Set Function Generator to $1V_{pk}$ and $1kHz$
3. Replaced the $1.3k\Omega$ resistor with the 20Ω resistor after >3 seconds
4. Measured and recorded:
 - a. I_{tot}
 - b. $V_{20\Omega}$
 - c. V_{FG} (function generator voltage)
5. Repeated these measurements for $2kHz$, $3kHz$, $4kHz$, and $5kHz$
6. Repeated 1-5 for the circuit in **Figure 4**





Procedure: Formulas and theorems

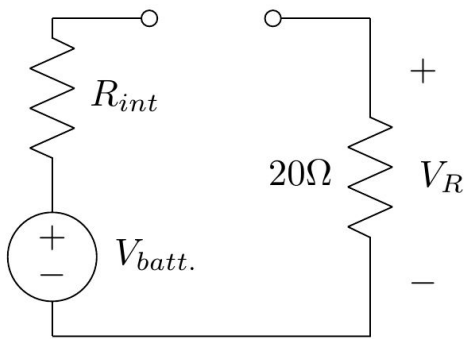- Superposition theorem
 - To suppress a *voltage* source, replace it with a *short* circuit.
 - By solving these two circuits, we get the equation:



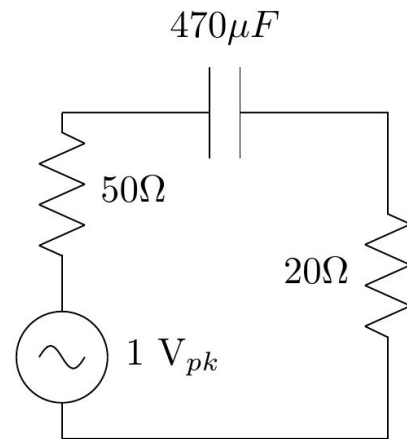
$$R_1 = \frac{V_{FG} - V_R}{I_{tot}} \text{ (without battery)}$$
$$R_{int} = \frac{V_{FG} - V_R}{I_{tot}} - R_1$$



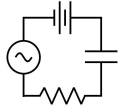


Procedure: Calculations

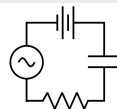1. The capacitor opened the circuit with just DC source
2. Applied Kirchhoff's voltage law with the circuit with the battery voltage blocked
3. Calculated the total impedance from the known resistances
4. Used Ohm's law to get the voltage through the total known impedance
5. Derived from there the resistor needed to fulfill Kirchhoff's law





Results

	Without battery			With battery		
f (Hz)	V_R (V)	I_{tot} (mA)	R_1 (Ω)	V_R (V)	I_{tot} (mA)	R_{int} (Ω)
1000	0.19530	9.86	51.9074	0.19484	9.83	0.2052
2000	0.19537	9.88	51.7952	0.19501	9.83	0.3001
3000	0.19535	9.89	51.7449	0.19504	9.83	0.3474
4000	0.19535	9.89	51.7449	0.19514	9.83	0.3372
5000	0.19533	9.89	51.7469	0.19515	9.83	0.3342

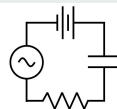


Results: Rin plot

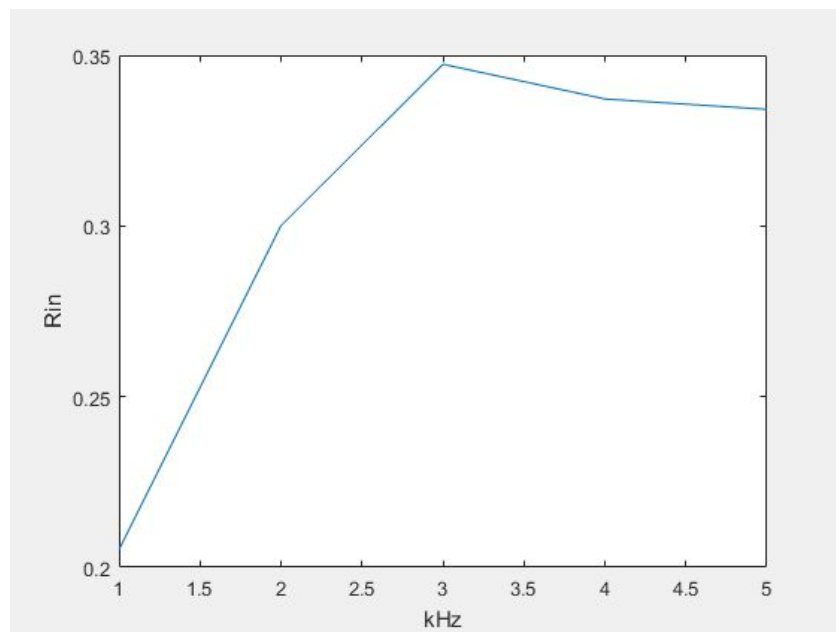

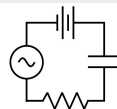

Results: Precision and accuracy

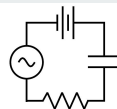- Mean of the R_{in} was 0.30482Ω
- The value of the resistance matched our expectations
- We could not measure the accuracy without the real value of the internal resistance
- The variance of the R_{in} was 0.0034Ω
- The data was precise regardless of the accuracy



Conclusions

- The results were consistent
- The samples that were taken matched our expectations
- Possible inductance in the battery as R_{in} changed with the frequency
- Possible errors due to impedance in wires used



References

- <https://www.sciencedirect.com/science/article/pii/S1388248109005980>
- <https://patentimages.storage.googleapis.com/1f/dc/29/7eb23147dc4239/US20070194791A1.pdf>
- <https://literature.cdn.keysight.com/litweb/pdf/5989-8926EN.pdf?id=1456157>