

Chapter 8: RLC Circuits

Natural Response:

$$\alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

① $\omega_0^2 < \alpha^2$ overdamped

~~$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$~~

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

② $\omega_0^2 > \alpha^2$ underdamped

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

③ $\omega_0^2 = \alpha^2$ critically damped

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

Step Response:

$$\left\{ \begin{aligned} i(t) &= i_f + \left\{ \begin{array}{l} \text{Function of the same} \\ \text{form as natural response} \end{array} \right\} \end{aligned} \right.$$

$$\left\{ \begin{aligned} v(t) &= v_f + \left\{ \begin{array}{l} \text{function of the same} \\ \text{form as natural response} \end{array} \right\} \end{aligned} \right.$$

Chap. 7: R-L & R-C Circuits

First-order RL & RC Circuits

General Solution for Natural & Step Response of RL & RC circuits is given by:

$$x(t) = x_f + [x(t_0) - x_f] e^{-(t-t_0)/\tau}$$

Note: t_0 may be equal to zero or some other stated time.

R-L Circuit: $\tau = \frac{L_{eq}}{R_{Thermin}}$

R-C circuit: $\tau = R_{Thermin} C_{eq}$

$$v_C(0^+) = v_C(0^-) \quad \& \quad i_L(0^+) = i_L(0^-)$$

Energy stored in Capacitors:

$$W_C = \frac{1}{2} C V_C^2$$

Energy stored in Inductors:

$$W_L = \frac{1}{2} L I_L^2$$

$$i_C = C \frac{dv_C}{dt}, \quad v_L = L \frac{di_L}{dt}$$

$$P = i \times v$$

Ohm's Law: $V = IR$ or $I = \frac{V}{R}$

Power: $P = I^2 R = I \cdot V = \frac{V^2}{R}$

Nodal Analysis: Application of Kirchhoff Current Law (KCL)

Mesh Analysis: Application of Kirchhoff Voltage Law (KVL)