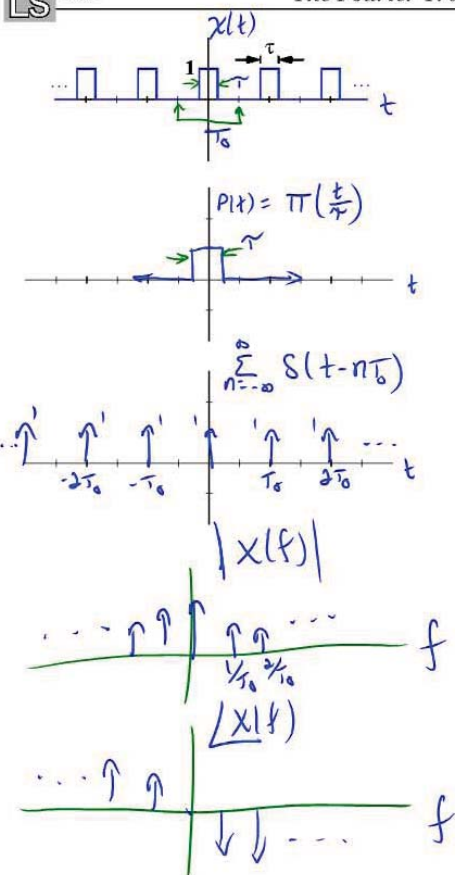


$$a(t) \delta(t-t_0) = a(t_0) \delta(t-t_0)$$

$$a(t) * \delta(t-t_0) = a(t-t_0)$$



$$X(f) = \mathfrak{F} \left\{ \sum_{n=-\infty}^{\infty} \Pi \left(\frac{t-nT_0}{\tau} \right) \right\}$$

$$x(t) = p(t) * \sum_{n=-\infty}^{\infty} \delta(t-nT_0)$$

$$= \sum_{n=-\infty}^{\infty} \underbrace{p(t) * \delta(t-nT_0)}_{p(t-nT_0)}$$

$$X(f) = \mathfrak{F} \{ x(t) \} = \mathfrak{F} \left\{ p(t) * \sum_{n=-\infty}^{\infty} \delta(t-nT_0) \right\}$$


$$= \underbrace{\mathfrak{F} \{ p(t) \}}_{p(f)} * \underbrace{\mathfrak{F} \left\{ \sum_{n=-\infty}^{\infty} \delta(t-nT_0) \right\}}_{\frac{1}{T_0} \sum_{k=-\infty}^{\infty} \delta(f - \frac{k}{T_0})}$$

$$= \text{sinc}(fT_0) \cdot \frac{1}{T_0} \sum_{k=-\infty}^{\infty} \delta(f - \frac{k}{T_0})$$

$$X(f) = \text{sinc}(fT_0) \cdot \frac{1}{T_0} \sum_{k=-\infty}^{\infty} \delta(f - \frac{k}{T_0})$$

$$= \sum_{k=-\infty}^{\infty} \left[\frac{T_0}{T_0} \text{sinc}(fT_0) \right] \delta(f - \frac{k}{T_0}) = \sum_{k=-\infty}^{\infty} \frac{T_0}{T_0} \text{sinc} \left(\frac{k}{T_0} T_0 \right) \delta(f - \frac{k}{T_0})$$

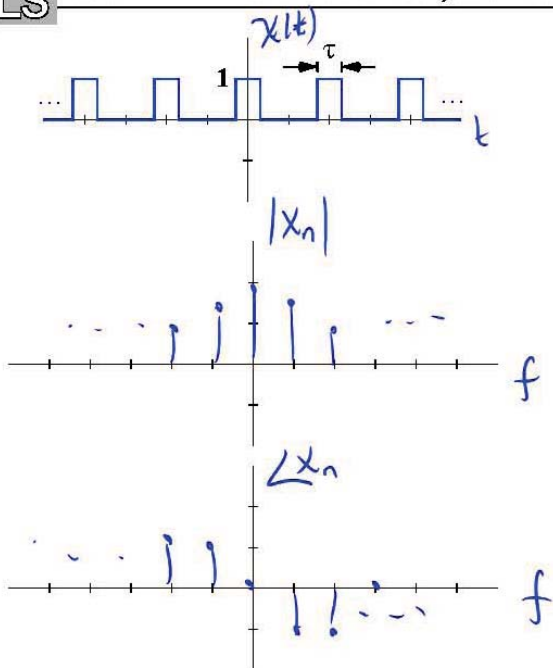$f - \frac{k}{T_0} = 0 \Rightarrow f = \frac{k}{T_0}$



$$x(t) = \sum_{n=-\infty}^{\infty} X_n e^{jn\omega_0 t}$$

$$X_n = \frac{1}{T_0} \int_{T_0} x(t) e^{-jn\omega_0 t} dt$$

$$X_n = \text{WEIGHT OF S PINE IN } X(f)$$

$$\text{AT } f = \frac{n}{T_0}$$

❖ Find the signal $h(t)$ defined by the DE

ASSUME ALL INITIAL ARE ZERO.

$$RC \frac{d}{dt} h(t) + h(t) = \delta(t)$$

$$h(t) = \frac{1}{RC} e^{-\frac{1}{RC}t} u(t)$$

$$\mathcal{F}\left\{RC \frac{d}{dt} h(t) + h(t)\right\} = \mathcal{F}\{\delta(t)\}$$

$$RC \mathcal{F}\left\{\frac{d}{dt} h(t)\right\} + \mathcal{F}\{h(t)\} = \mathcal{F}\{\delta(t)\}$$

$$(j2\pi f) H(f) + H(f) = 1$$


LINEARITY THEOREM

$$RC(j2\pi f) H(f) + H(f) = 1$$

$$H(f) = \frac{1}{1 + j2\pi f RC} = \frac{1}{RC} \left[\frac{1}{\frac{1}{RC} + j2\pi f} \right]$$

❖ Find the impulse response for the circuit shown.

$$i(t) = C \frac{d}{dt} v(t)$$

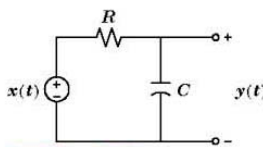



METHOD #1: FIND SYSTEM I/O, SOLVE TO FIND $h(t)$

$$RC \frac{d}{dt} y(t) + y(t) = x(t)$$

$$\text{FIND } h(t) \text{ BY SOLVING } RC \frac{d}{dt} h(t) + h(t) = \delta(t)$$


ASSUME I.C. ARE ZERO
SEE PREVIOUS SLIDE
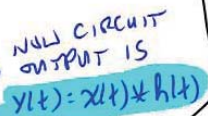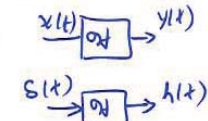
$$h(t) = \frac{1}{RC} e^{-\frac{1}{RC}t} u(t)$$



NEW CIRCUIT OUTPUT IS $y(t) = x(t) * h(t)$

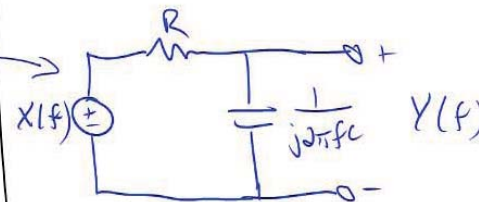METHOD #2: CONVERT CIRCUIT INTO THE FREQ. DOMAIN COMPONENT AND SOLVE.



VOLTAGE DIVISION

$$Y(f) = X(f) \left[\frac{\frac{1}{j2\pi f C}}{R + \frac{1}{j2\pi f C}} \right] (j2\pi f C)$$

$$\frac{Y(f)}{X(f)} = \frac{1}{1 + j2\pi f RC} = H(f)$$

$$Y(f) = X(f) H(f)$$

$$\frac{Y(f)}{X(f)} = H(f)$$

ASIDE

$$i(t) \rightarrow \frac{R}{+v(t)}$$

$$v(t) = i(t) R$$

$$\mathcal{F}\{v(t)\} = \mathcal{F}\{i(t) R\}$$

$$V(f) = I(f) R$$

$$R = \frac{V(f)}{I(f)}$$

$$i(t) \rightarrow \frac{C}{+v(t)}$$

$$i(t) = C \frac{d}{dt} v(t)$$

$$\mathcal{F}\{i(t)\} = \mathcal{F}\left\{C \frac{d}{dt} v(t)\right\}$$

$$I(f) = C(j2\pi f) V(f)$$

$$\frac{V(f)}{I(f)} = \frac{1}{j2\pi f C} = Z(f)$$

$$i(t) \rightarrow \frac{L}{+v(t)}$$

$$v(t) = L \frac{d}{dt} i(t)$$


$$V(f) = L(j2\pi f) I(f)$$

$$\frac{V(f)}{I(f)} = j2\pi f L = Z(f)$$

- ❖ Find the **impulse response** for the circuit shown.



TRY THIS ON YOUR OWN

$$i(t) = C \frac{d}{dt} v(t)$$

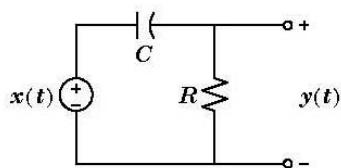

- ❖ Find the **impulse response** for the circuit shown.

$$i(t) = C \frac{d}{dt} v(t)$$

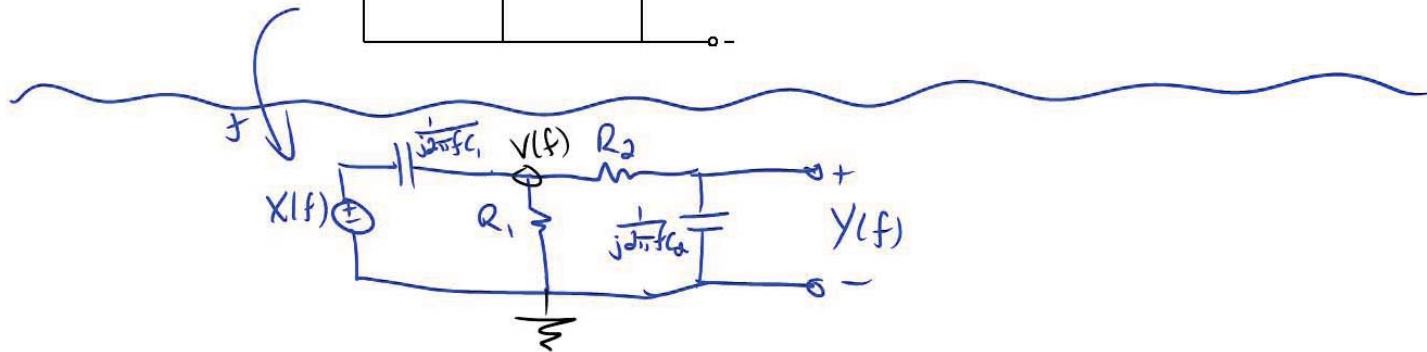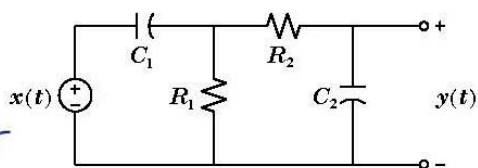

FIND $V(f)$ USING NODAL ANALYSIS, THEN USE VOLTAGE DIVISION TO RELATE $V(f)$ TO $Y(f)$.


- ❖ An LTI system with impulse $h(t)$ has **Transfer Function**

$$H(f) = \mathcal{F}\{h(t)\}$$

Note: $H(f)$ is generally a complex function

REAL SIGNAL
GENERALLY BE COMPLEX

KNOW THIS!

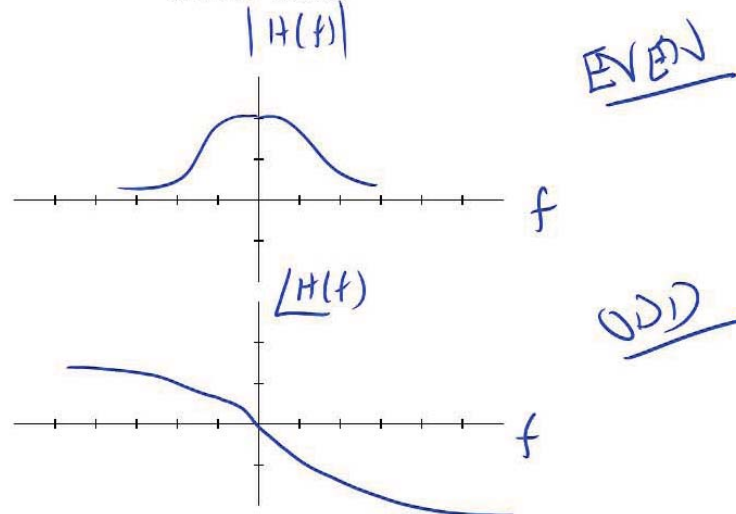

- ❖ Find $y(t)$ for an LTI system with Transfer Function $H(f)$ and with input

$$x(t) = A \cos(2\pi f_0 t + \theta)$$

LTI

$x(t) \rightarrow \boxed{H(f)} \rightarrow y(t)$

$y(t) = x(t) * h(t)$

$y(t) = A |H(f_0)| \cos[2\pi f_0 t + \theta + \angle H(f_0)]$

